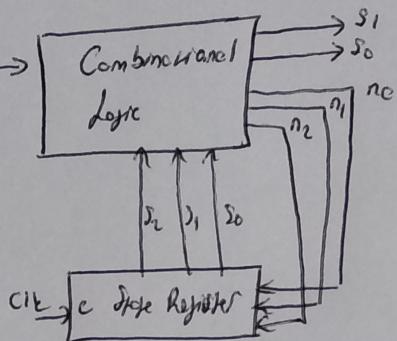


Step-1

Step-2 A, B

- 3 bit state register (Parallel) \rightarrow
- Output S_2, S_1, S_0
- Next state n_2, n_1, n_0




Step 2 C

| S_2 | S_1 | S_0 | B | n_2 | n_1 | n_0 | S_1 | S_0 |
|-------|-------|-------|---|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 |


Step-2 D

$$\begin{aligned}
 n_2 &= S_2' S_1 S_0 B' + S_2 S_1' + S_2 S_0' + S_2 B \\
 n_1 &= S_1 S_0' + S_1 B + S_2 S_0 B + S_2' S_1 S_0 B' \\
 n_0 &= S_0' B + S_2' B + S_1 B + S_2 S_1' S_0 B' \\
 S_1 &= S_1 S_0' + S_2 S_1' + S_2' S_1 S_0 \\
 S_0 &= S_1 \text{ XOR } S_0
 \end{aligned}$$

6-)

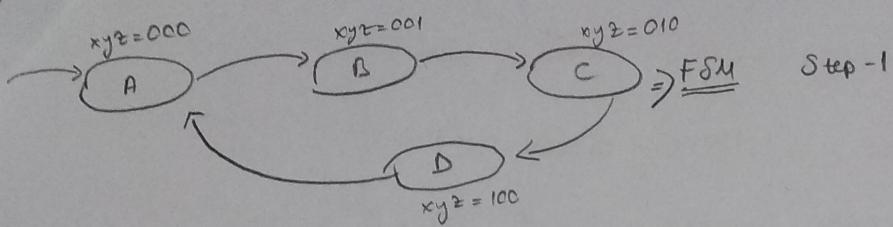

Step 2-A-B

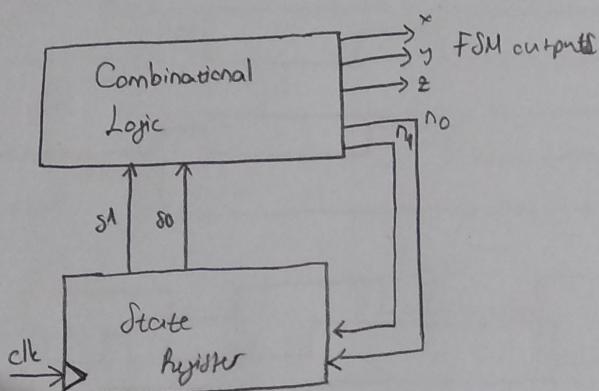 \approx 2 bit state register (4 states "A,B,C,D")- Output x, y, z - Next state signals n_1, n_0 

Step 2-C

| Input | | Output | | | | |
|-------|-------|--------|-----|-----|-------|-------|
| s_1 | s_0 | x | y | z | n_1 | n_0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

Step 2-D

Implement Combinational Logic


$$n_0 = s_1's_0' + s_1s_0' = s_0'(s_1 + s_1') = s_0'$$

$$n_1 = s_1's_0 + s_1s_0'$$



$$z = s_1's_0$$

$$y = s_1s_0'$$

$$x = s_1s_0$$

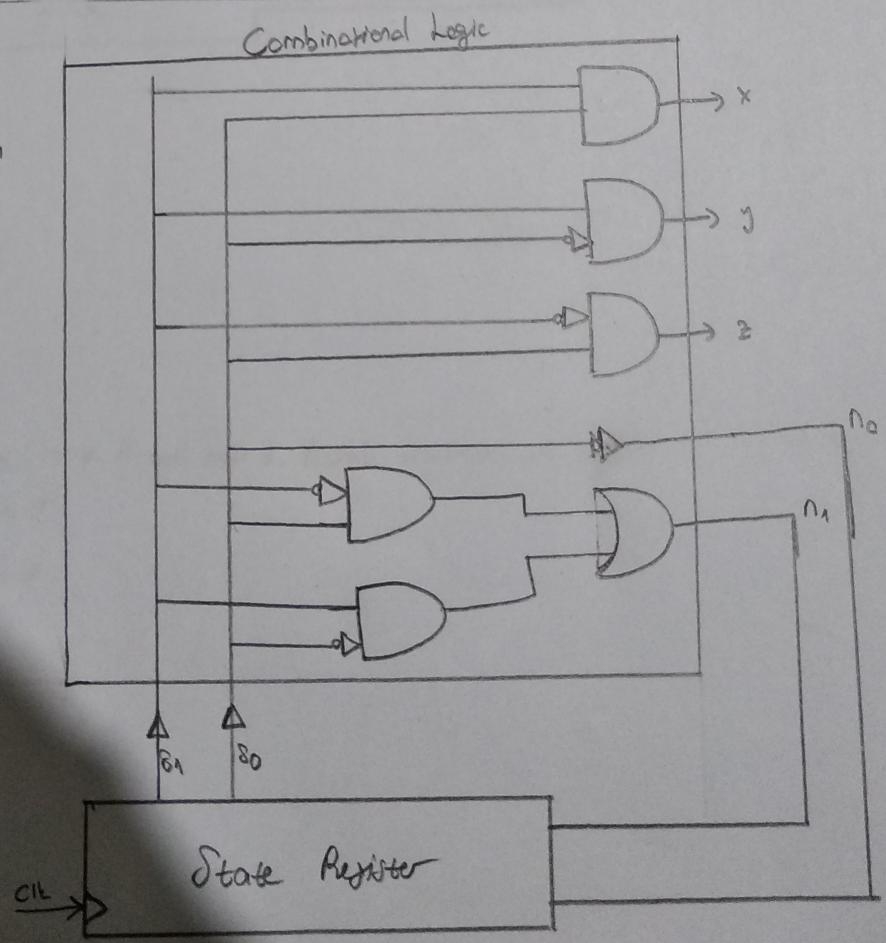

- 1 -
- $P = 1/50\text{kHz} = 1/50 \times 10^3 \text{s} = 1/500 \text{ms} = 0.02 \text{ms} = 20 \text{ns}$
 - $P = 1/300\text{MHz} = 1/300 \times 10^6 \text{s} = 1/300 \mu\text{s} = 3.33 \times 10^{-3} \mu\text{s} = 3.33 \text{ ns}$
 - $P = 1/3.46\text{Hz} = 1/3.46 \times 10^9 \text{s} = 1/3.46 \text{ ns} = 0.294 \text{ ns} = 294 \text{ ps}$
 - $P = 1/106\text{Hz} = 1/106 \times 10^9 \text{s} = 1/106 \text{ ns} = 0.1 \text{ ns} = 100 \text{ ps}$
 - $P = 1/1\text{THz} = 1/10^{12} \text{s} = 1 \text{ ps}$

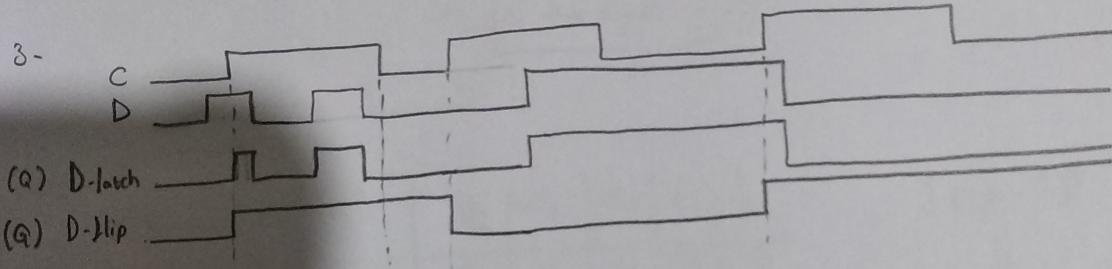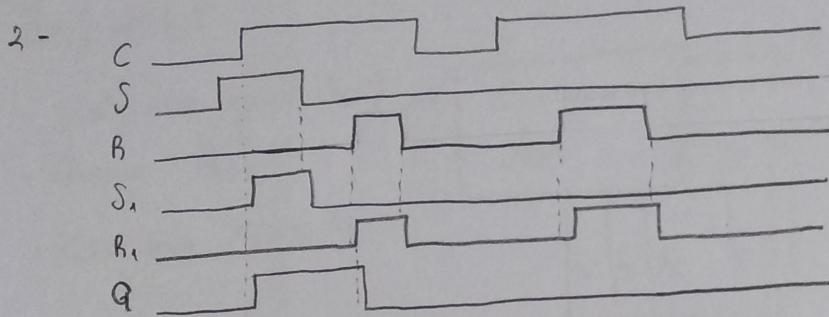

- 4 -
- Number of bits = $\log_2 4 = 2$
 - Number of bits = $\log_2 8 = 3$
 - " = $\log_2 9 = 3.18 \Rightarrow 4$
 - " = $\log_2 23 = 4.52 \Rightarrow 5$
 - " = $\log_2 900 = 9.1 \Rightarrow 10$

- 5 -) Assume that there are two states, state A and state B. Possible transitions are s-A to s-B and sB to s-A.
 Thus the possible transitions $2 \times 1 = 2$
 so possible transitions $n \cdot (n-1) \neq$